



Name:-

SARDAR MURAAD WAHEED

Roll No:-

2024-CET-18

Semester:-

2ND SEMESTER

Subject:-

DLD

Submitted To:-


ENGR.SIDRA RAFIQUE

Submitted Date:-



04-JUN-2025

Lab 4

Experiment on EWB

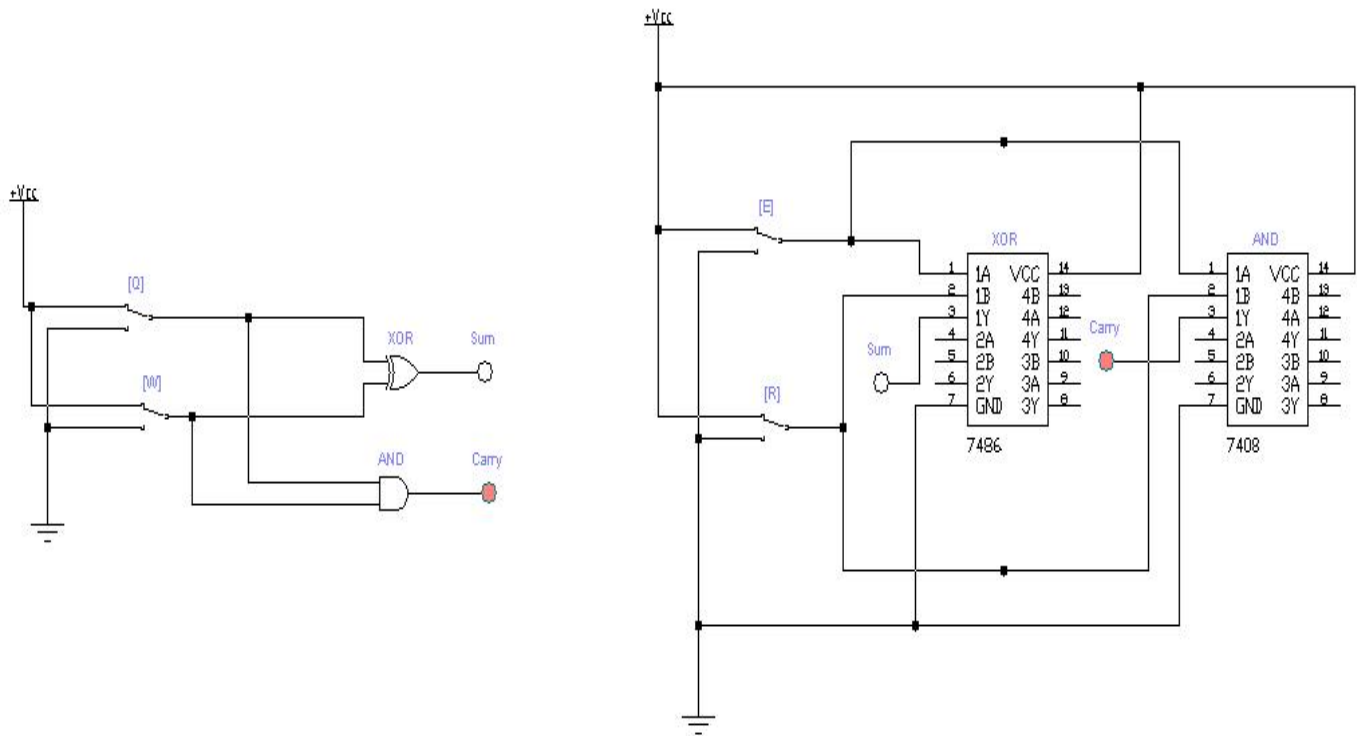


Carry Output

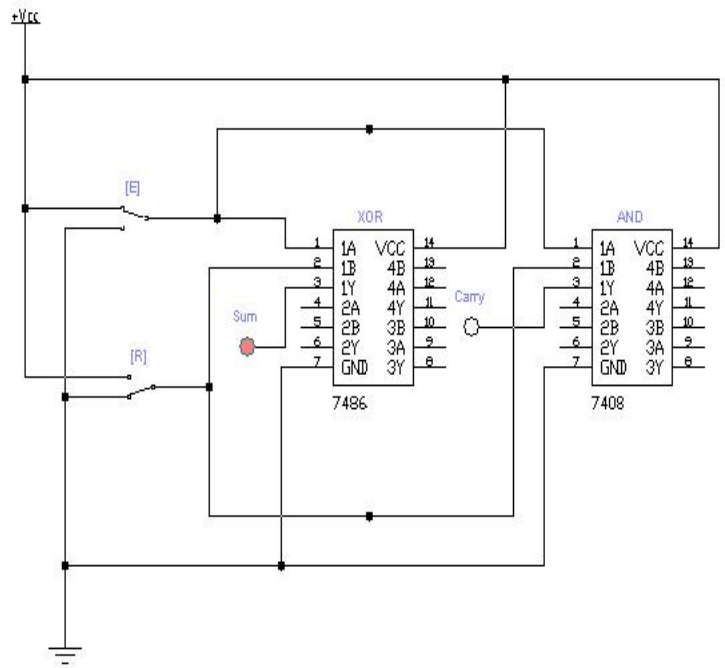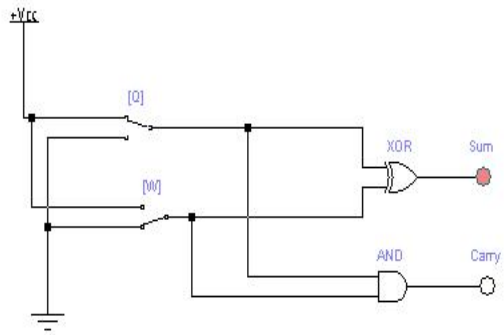

Sum Output

Experiment on Hardware

Simple Circuit Implementation

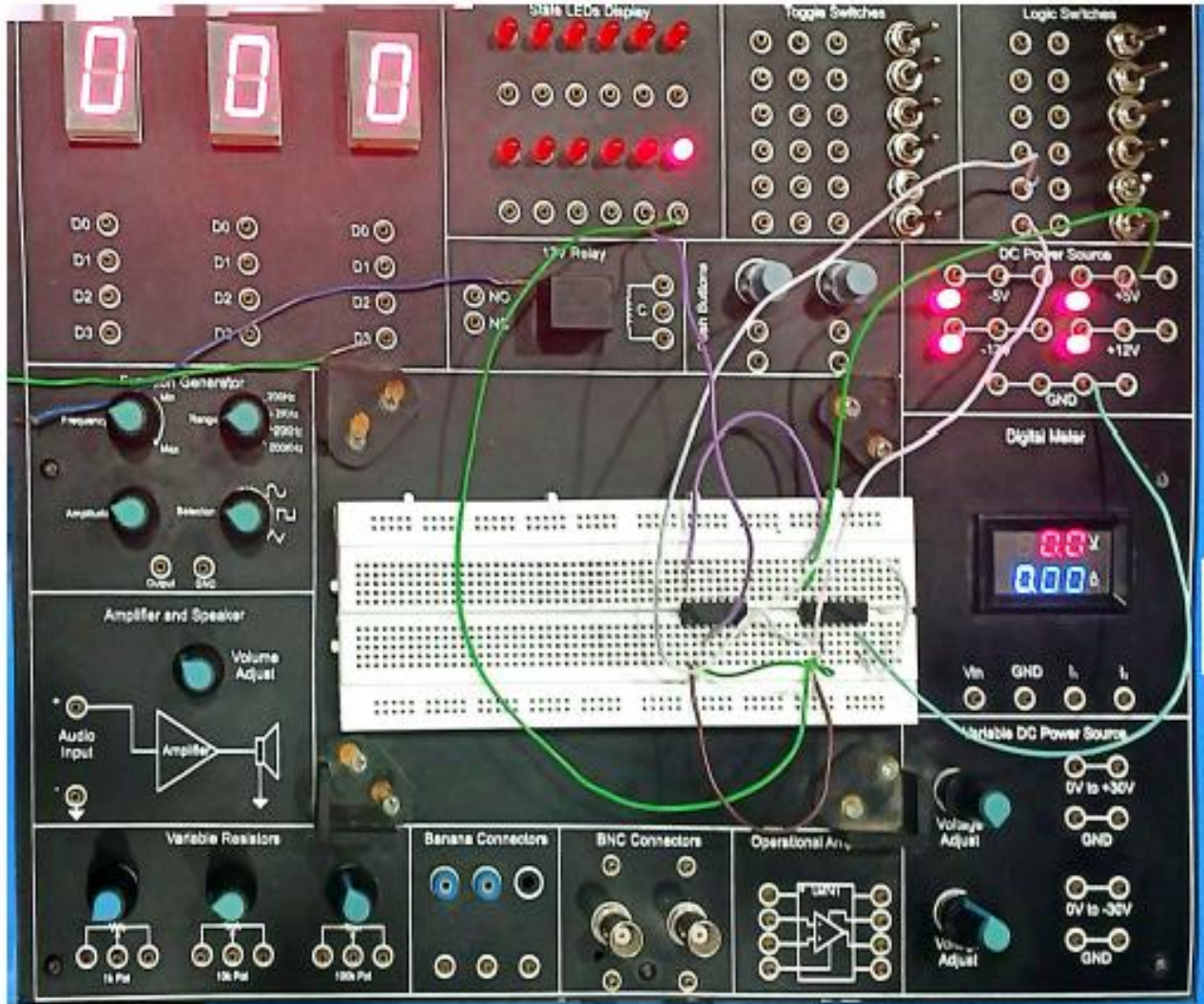

- Circuit shows the implementation of Half Adder using ICs of XOR and AND.

Complicated Circuit Implementation

