 


Name:-Murad Waheed
Roll No:-18-CET-2024
Group:-Computer Engineering Technology
Subject:-DLD

Circuit No1:-

$$F = (A + B)(A + C)$$



Inputs:

Three input switches labeled A, B, and C on the left side.

Logic Gates:

Two OR gates:

- First OR gate has inputs A and B.
- Second OR gate has inputs A and C.

One AND gate:

- Takes the outputs of the two OR gates as its input.
- Output of the AND gate represents the final function
 $f = (A + B)(A + C)$.

Output:

- The final output from the AND gate is connected to an output probe (highlighted in red), which likely indicates the current logic level (HIGH/LOW).

Logic Converter Tool:

- Located below the circuit.
- Displays the truth table for all combinations of A, B, and C.
- Outputs the result of the logic function f for each input combination.
- It confirms that the output matches the expression $(A + B)(A + C)$.


Truth Table Of This Gate:

| A | B | C | $F = (A+B)(A+C)$ |
|---|---|---|------------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |

| | | | |
|---|---|---|---|
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Circuit No2:-

$$F = AB(BC + AC)$$

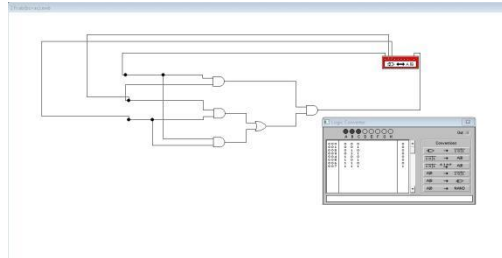

1. Inputs:

Three input switches labeled A, B, and C (left side of the circuit).

2. Gate Structure:

First AND Gate:

Inputs: A and B

Output: AB

Second AND Gate:

Inputs: B and C

Output: BC

Third AND Gate:

Inputs: A and C

Output: AC

OR Gate:

Inputs: BC and AC

Output: BC + AC

Final AND Gate:

Inputs: AB and (BC + AC)

Output: $f = AB(BC + AC)$

3. Output:


The final output from the last AND gate is connected to an output probe (highlighted in red), which likely reflects the current binary state (logic high/low).

Truth Table:

| A | B | C | F= AB(BC + AC) |
|---|---|---|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Circuit No3:-

$$Z = A + (BC) + (AC)$$

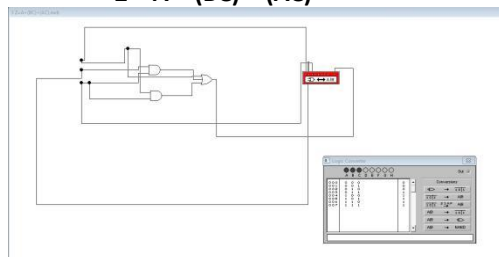

1. Inputs:

Three input switches:

A, B, and C (on the left side of the circuit).

2. Logic Gates and Connections:

First AND Gate:

Inputs: B and C

Output: BC

Second AND Gate:

Inputs: A and C

Output: AC

OR Gate:

Inputs: BC, AC, and A

Output: $Z = A + BC + AC$

3. Output:


The final output from the OR gate is connected to an output probe (highlighted in red) to show the logic state of Z.

Truth Table:

| A | B | C | $Z=A+(BC)+(AC)$ |
|---|---|---|-----------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Circuit No4:-

$$F = x'y + yz' + YZ + XY'Z'$$

 

- **NOT Gates:**

- A NOT gate inverts x to produce x'
- A NOT gate inverts z to produce z'
- A NOT gate inverts y to produce y'

- **AND Gates:**

- The first AND gate takes x' and y to produce x'y
- The second AND gate takes y and z' to produce yz'
- The third AND gate takes y and z to produce yz
- The fourth AND gate takes x, y, and z' to produce xy'z'

- **OR Gate:** The outputs of the four AND gates (x'y, yz', yz, and xy'z') are fed into an OR gate to compute the final expression $F = x'y + yz' + yz + xy'z'$.


- **Output:** The output of the OR gate is the final function F.

Truth Table:

| A | B | C | $F = x'y + yz' + YZ + XY'Z'$ |
|---|---|---|------------------------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Circuit No5:-

$$F = x'y + yz' + YZ + XY'Z'$$

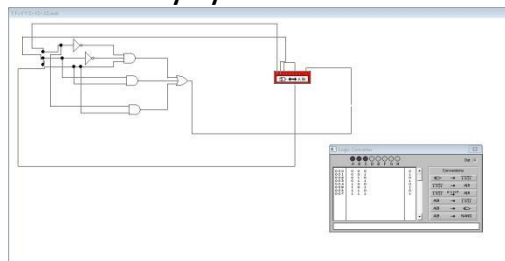

- **Inputs:** The circuit has three inputs: x , y, and z.
- **NOT Gates:**
 - A NOT gate inverts x to produce x' .
 - A NOT gate inverts y to produce y'
- **AND Gates:**
 - The first AND gate takes x' , y'', and z to produce x'y'z
 - The second AND gate takes y and z to produce yz.
 - The third AND gate takes x and z to produce xz.
- **OR Gate:** The outputs of the three AND gates (x'y'z , yz, and xz) are fed into an OR gate to compute the final expression $F=x'y'z+yz+xz$
- **Output:** The output of the OR gate is the final function F.

Truth Table:

| A | B | C | $F = x'y + yz' + YZ + XY'Z'$ |
|---|---|---|------------------------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |